

Intro to Quantum Computing : ECES622 - Winter 2012

80/80

Homework 2
23 January 2012
Hua Li, Kevin Pasko, Allen Welch

1.

$$A \text{ AND } 0 = 0$$

A	0	A*0
0	0	0
1	0	0

$$A + 1 = 1$$

A	1	A+1
0	1	1
1	1	1

10/60

$$A + (A \text{ AND } B) = A$$

A	B	AB	A+AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

$$A + ((\sim A) \text{ AND } B) = A + B$$

A	A'	B	A'B	A+A'B	A+B
0	1	0	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	0	1	0	1	1

2.

AB	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	fa	fb	fc	fd	fe	ff
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

$$F9 = (\sim A)(\sim B) + AB$$

A	A'	B	B'	A'B'	AB	A'B'+AB	f9
0	1	0	1	1	0	1	1
0	1	1	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	0	1	1	1

20/30

$$F6 = A(\sim B) + (\sim A)B$$

A	A'	B	B'	AB'	A'B	AB'+A'B	f6
0	1	0	1	0	0	0	0
0	1	1	0	0	1	1	1
1	0	0	1	1	0	1	1
1	0	1	0	0	0	0	0

$$F2 = A(\sim B)$$

A	B	B'	AB'	f2
0	0	1	0	0
0	1	0	0	0
1	0	1	1	1
1	1	0	0	0

3.

a	b	CarryIn	Sum	CarryOut
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

a	b'	CarryIn'	ab'CarryIn'
0	1	1	0
0	1	0	0
0	0	1	0
0	0	0	0
1	1	1	1
1	1	0	0
1	0	1	0
1	0	0	0

a	a'	b	b'	CarryIn	CarryIn'
0	1	0	1	0	1
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	0	1	0
1	0	0	1	0	1
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	0	1	0

a	b	CarryIn	abCarryIn
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

a'	b'	CarryIn	a'b'CarryIn
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	0
0	1	1	0
0	0	0	0
0	0	1	0

a'	b	CarryIn	a'bCarryIn
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0

a'	b	CarryIn'	a'bCarryIn'
1	0	1	0
1	0	0	0
1	1	1	1
1	1	0	0
0	0	1	0
0	0	0	0
0	1	1	0
0	1	0	0

a	b	CarryIn'	abCarryIn'
0	0	1	0
0	0	0	0
0	1	1	0
0	1	0	0
1	0	1	0
1	0	0	0
1	1	1	1
1	1	0	0

a	b	CarryIn	abCarryIn
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

✓ W

$$\text{Sum} = a'b'\text{CarryIn} + a'b\text{CarryIn}' + ab'\text{CarryIn}' + ab\text{CarryIn}$$

a'b'CarryIn	a'bCarryIn'	ab'CarryIn'	abCarryIn	a'b'CarryIn+a'bCarryIn'+ab'CarryIn'+abCarryIn	Sum
0	0	0	0	0	0
1	0	0	0	1	1
0	1	0	0	1	1
0	0	0	0	0	0
0	0	1	0	1	1
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	1	1	1



$$\text{CarryOut} = a'b\text{CarryIn} + ab'\text{CarryIn} + ab\text{CarryIn}' + ab\text{CarryIn} \quad \checkmark \quad W$$

a'bCarryIn	ab'CarryIn	abCarryIn'	abCarryIn	a'bCarryIn+ab'CarryIn+abCarryIn'+abCarryIn	CarryOut
0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
1	0	0	0	1	1
0	0	0	0	0	0
0	1	0	0	1	1
0	0	1	0	1	1
0	0	0	1	1	1




$$\begin{aligned}
 \text{CarryOut} &= a'b\text{CarryIn} + ab'\text{CarryIn} + ab\text{CarryIn}' + ab\text{CarryIn} \\
 &= a'b\text{CarryIn} + ab'\text{CarryIn} + ab\text{CarryIn}' + ab\text{CarryIn} + ab\text{CarryIn} + ab\text{CarryIn} \\
 &= (a'b\text{CarryIn} + ab\text{CarryIn}) + (ab'\text{CarryIn} + ab\text{CarryIn}) + (ab\text{CarryIn}' + ab\text{CarryIn}) \\
 &= b(a'\text{CarryIn} + a\text{CarryIn}) + a(b'\text{CarryIn} + b\text{CarryIn}) + ab(\text{CarryIn}' + \text{CarryIn}) \\
 &= b(a' + a)\text{CarryIn} + a(b' + b)\text{CarryIn} + ab(1) \\
 &= b(1)\text{CarryIn} + a(1)\text{CarryIn} + ab \\
 &= b\text{CarryIn} + a\text{CarryIn} + ab
 \end{aligned}$$

✓ W

4. Programmable QCA AND Gate

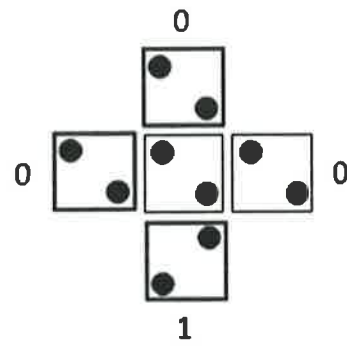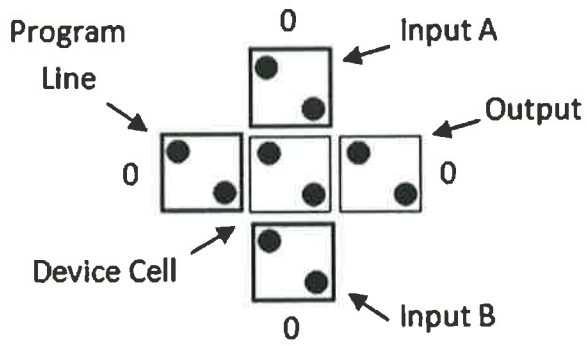

10

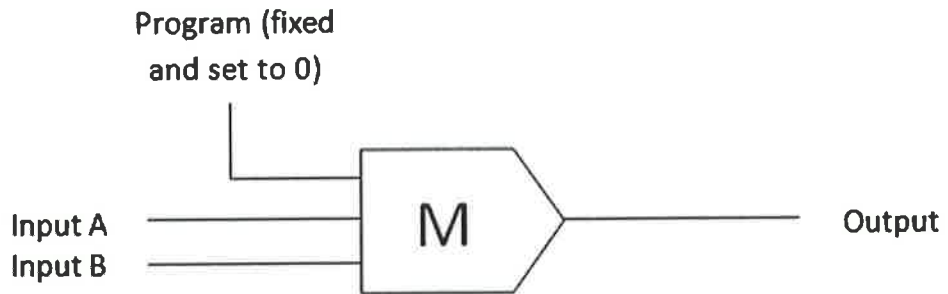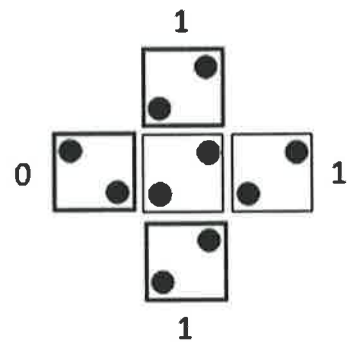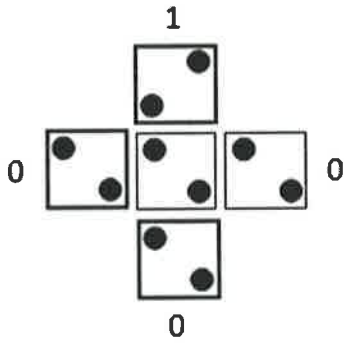

Program	A	B	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1